

NUMERICAL METHODS FOR ENGINEERING ASSIGNMENT.

FET651

Group 6 membres

Full Name	Matriculation number	<u>Speciality</u>
ABANDA PACILIA COLETTE	FE20P070	NETWROK
NJIKE TCHAPTCHET MAEVA DORCAS	FE20P072	NETWORK
LOUMOU BALATA PATRICK PASCAL	FE20P103	TELECOM
TCHOUASSEU KAMNANG BRICE RUDY	FE20P069	NETWORK
KANGNUO CHENUI NIXON	FE20P076	NEWTORK

Calculation

CH.3- System of linear equations

Goal:

Solve a system of linear equations with varying free parameters.

Problem:

Consider the following circuit.

1. Use Kirchhoff laws of current and voltage, obtain the system of equations that satisfy the currents.
2. The voltage U (in volts) is varying in the interval $[200, 240]$ by steps of 1 volt. Using Matlab or Python, write a code that solves the problem.
 - Display the currents for $U=240$ V.
 - Plot the currents as functions of U .

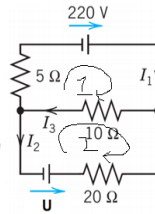


Figure 1: question

Solution

From loop 1, using kirchoff's law, traversing the circuit in the direction of current, we have;

- $I_3 = I_1 + I_2$ _____ 1
- $-5I_1 - 10I_3 + 220 = 0$

→ $+5I_1 + 10I_3 = 220$ _____ 2

- $10I_3 + 20I_2 - U = 0$

→ $10I_3 + 20I_2 = U$ _____ 3

This implies that $-I_1 - I_2 + I_3 = 0$

$5I_1 + 0I_2 + 10I_3 = 0$

$0I_1 + 20I_2 + 10I_3 = 0$

Expressed in matrix form as;

$$\begin{pmatrix} 0 \\ 220 \\ u \end{pmatrix} = \begin{pmatrix} -1 & -1 & 1 \\ 5 & 0 & 10 \\ 0 & 20 & 10 \end{pmatrix} \begin{pmatrix} I(1) \\ I(2) \\ I(3) \end{pmatrix}$$

Python code

```
import matplotlib
import matplotlib.pyplot as plt
import numpy as np

y1= []
y2= []
y3= []
b=[]
#  $13 - 11 - 12 = 0$  .....eq1
#  $511 + 1013 - 220 = 0$ .....eq2
#  $1013 + 2012 - u = 0$ .....eq3
det= np.linalg.det([[ -1 , -1 , 1],[5, 0 ,10], [0, 20,10]])
for u in range(200, 241):
    b.append(u)
for u in range (200,241):
    det1=np.linalg.det([[0 , -1 , 1],[220, 0 ,10], [u, 20,10]])
    i1=det1/det
    y1.append(i1)
for u in range (200,241):
    det2=np.linalg.det([[ -1 , 0 , 1],[5, 220,10], [0,u,10]])
    i2=det2/det
    y2.append(i2)
for u in range (200,241):
    det3=np.linalg.det([[ -1 , -1 , 0],[5, 0 ,220], [0, 20,u]])
    i3=det3/det
    y3.append(i3)
plt.plot(b, y1,label = "i 1")
plt.plot(b, y2,label = "i 2")
plt.plot(b, y3,label = "i 3")
plt.xlabel('U (voltage)')
plt.ylabel('I (Current)')
plt.legend()
plt.show()
```

Output results

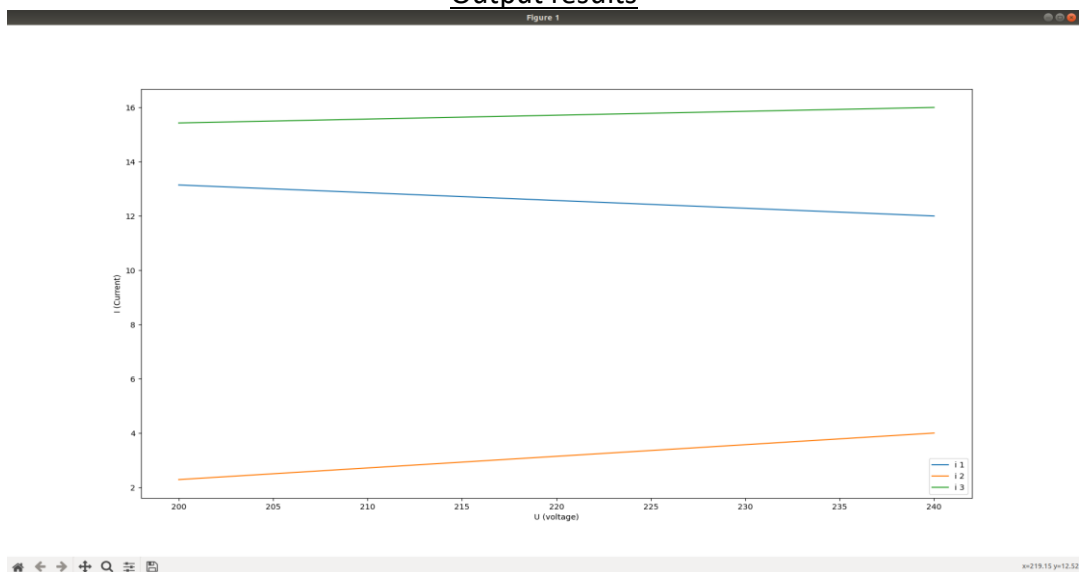


Figure 2: Output result